SCI6-CIRCUITS-01 - YEAR 6 SCIENCE TEST: CIRCUITS (MULTIPLE CHOICE)

Circle one letter for each question.

1. What does a circuit need to work?
A) a gap B) a complete loop C) two batteries D) a switch

2. Which material lets electricity through?
A) plastic B) wood C) copper D) glass

3. What does a switch do?
A) stores electricity B) makes the bulb brighter C) breaks or completes the loop D) slows the current

4. What happens to two bulbs in a series circuit when one is removed?
A) both stay lit B) both go out C) the other gets brighter D) nothing changes

5. Which symbol stands for a bulb in a circuit diagram?
A) a zigzag line B) a circle with a cross C) two parallel lines D) a triangle

ANSWERS: 1-B, 2-C, 4-B

Total: 5 points.
GRADE BOUNDARIES: A: 5. B: 4. C: 3. D: 0-2.